

Circuits and Transforms

Pranav B*

CONTENTS

1	Definitions	1
2	Laplace Transform	1
3	Initial Conditions	3

Abstract—This manual provides a simple introduction to Transforms

1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of $g(t)$ is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

2 LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes $q_1 \mu C$. Then S is switched to position Q. After a long time, the charge on the capacitor is $q_2 \mu C$.

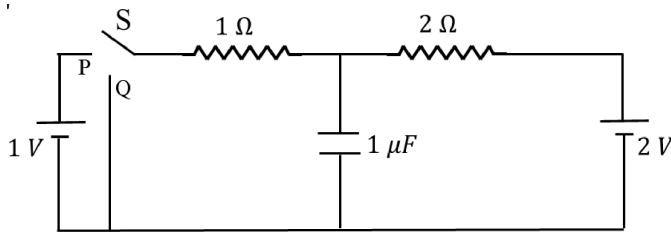


Fig. 2.1

2. Find q_1 .

Solution: : At steady state capacitor behaves like an open circuit. Assume current i flows

in the circuit in anti-clockwise direction, using KVL

$$-2 + 2i + i + 1 = 0 \quad (2.1)$$

$$\therefore i = \frac{1}{3}A \quad (2.2)$$

Assume V_C be voltage across the capacitor at that time,

$$\Rightarrow -2 + 2i = -V_C \quad (2.3)$$

$$\therefore V_C = \frac{4}{3}V \quad (2.4)$$

$$V_C = \frac{q_1}{C} \quad (2.5)$$

$$\Rightarrow q_1 = \frac{4}{3}\mu C \quad (2.6)$$

3. Show that the Laplace transform of $u(t)$ is $\frac{1}{s}$ and find the ROC.

Solution: :

$$\mathcal{L}[u(t)] = \int_{-\infty}^{\infty} u(t)e^{-st} dt \quad (2.7)$$

$$= \int_0^{\infty} e^{-st} dt \quad (2.8)$$

$$= \frac{1}{s} \quad (2.9)$$

ROC: $\text{Re}(s) > 0$

4. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{H}} \mathcal{L} \frac{1}{s+a}, \quad a > 0 \quad (2.10)$$

and find the ROC.

Solution: :

$$\mathcal{L}[e^{-at}u(t)] = \int_{-\infty}^{\infty} u(t)e^{-(s+a)t} dt \quad (2.11)$$

$$= \int_0^{\infty} e^{-(s+a)t} dt \quad (2.12)$$

$$= \frac{1}{s+a} \quad (2.13)$$

ROC: $\text{Re}(s) > -a$

5. Now consider the following resistive circuit transformed from Fig. 2.1 where

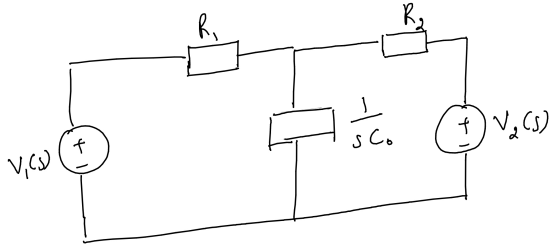


Fig. 2.2

$$u(t) \xleftrightarrow{\mathcal{H}} LV_1(s) \quad (2.14)$$

$$2u(t) \xleftrightarrow{\mathcal{H}} LV_2(s) \quad (2.15)$$

Find the voltage across the capacitor $V_{C_0}(s)$.

Solution: :

$$\mathcal{L}[V_1] = V_1(s) = \frac{1}{s} \quad (2.16)$$

$$\mathcal{L}[V_2] = V_2(s) = \frac{2}{s} \quad (2.17)$$

$$\mathcal{L}[C] = \frac{1}{Cs} \quad (2.18)$$

Using KVL,

$$i = i_1 + i_2 \quad (2.19)$$

$$\frac{-2}{s} + 2i_2 - \frac{i_1}{sC} = 0 \quad (2.20)$$

$$\frac{i_1}{sC} + i + \frac{1}{s} = 0 \quad (2.21)$$

$$\Rightarrow i_1(s) = -\frac{2}{s + \frac{3}{2C}} \quad (2.22)$$

$$\Rightarrow V_{C_0}(s) = \frac{i_1(s)}{sC} \quad (2.23)$$

$$= \frac{2}{C} \frac{1}{s(s + \frac{3}{2C})} \quad (2.24)$$

6. Find $v_{C_0}(t)$. Plot using python.

Solution: :Taking laplace inverse on both sides

of above equation

$$v_{C_0}(t) = \mathcal{L}^{-1} \left[\frac{2}{C} \frac{1}{s(s + \frac{3}{2C})} \right] \quad (2.25)$$

$$= \frac{4}{3} \mathcal{L}^{-1} \left[\frac{1}{s} - \frac{1}{s + \frac{3}{2C}} \right] \quad (2.26)$$

$$= \frac{4}{3} [1 - e^{-\frac{3}{2C}t}] u(t) \quad (2.27)$$

Run the following code

```
wget https://github.com/Pranavb060504/
SignalProcessing/blob/main/
circuits_and_transforms/vt.py
```

Use the following command in the terminal to run the code

```
python3 vt.py
```

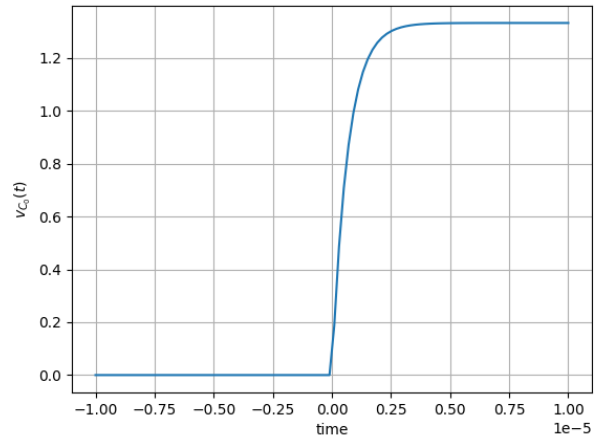


Fig. 2.3

7. Verify your result using ngspice.

Solution: : Run the following code

```
wget https://github.com/Pranavb060504/
SignalProcessing/blob/main/
circuits_and_transforms/C1.cir
```

Use the following command in the terminal to run the code

```
ngspice C1.cir
tran 0.0001ms 0.1ms
plot (V(Cin)-V(Cout))
```

3 INITIAL CONDITIONS

1. Find q_2 in Fig. 2.1.

Solution: : at $t=\infty$, capacitor is fully charged,

$$3i = 2 \quad (3.1)$$

$$i = \frac{2}{3}A \quad (3.2)$$

$$V_{C_0} = 2 - \frac{4}{3} = \frac{2}{3}V \quad (3.3)$$

$$q_2 = CV = \frac{2}{3}\mu C \quad (3.4)$$

2. Draw the equivalent s -domain resistive circuit when S is switched to position Q. Use variables R_1, R_2, C_0 for the passive elements.

3. $V_{C_0}(s) = ?$

Solution: :by junction law

$$i_1 + i_2 + i_3 = 0 \quad (3.5)$$

$$\frac{V_c}{R_1} + \frac{V_c - \frac{2}{s}}{R_2} + \frac{V_c - \frac{4}{3s}}{\frac{1}{sC_0}} = 0 \quad (3.6)$$

$$V_C(s) = \frac{\frac{1}{C} + \frac{4s}{3}}{s(s + \frac{3}{2C})} \quad (3.7)$$

4. $v_{C_0}(t) = ?$ Plot using python.

Solution: : Taking laplace inverse on both sides

$$v_{C_0}(t) = \mathcal{L}^{-1} \left[\frac{A}{s} + \frac{B}{s + \frac{3}{2C}} \right] \quad (3.8)$$

$$A = \frac{2}{3}, B = \frac{2}{3} \quad (3.9)$$

$$\therefore v_{C_0}(t) = \frac{2}{3}(1 + e^{\frac{-3}{2C}t})u(t) \quad (3.10)$$

Run the following code

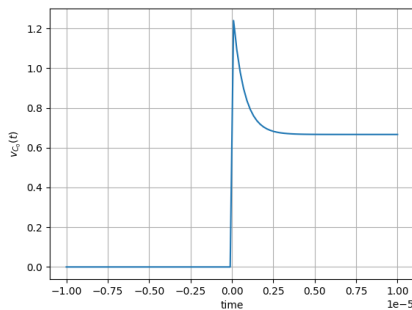


Fig. 3.1

Use the following command in the terminal to run the code

```
python3 vt1.py
```

5. Verify your result using ngspice.

Solution: : Run the following code

```
wget https://github.com/Pranavb060504/
SignalProcessing/blob/main/
circuits_and_transforms/C2.cir
```

Use the following command in the terminal to run the code

```
ngspice C2.cir
tran 0.0001ms 0.1ms
plot (V(Cin)-V(Cout))
```

6. Find $v_{C_0}(0^-)$, $v_{C_0}(0^+)$ and $v_{C_0}(\infty)$.

Solution: : for $t=0^-$ switch is still at P , so

$$V_C(0^-) = \frac{4}{3}V \quad (3.11)$$

from formula

$$V_C(0^+) = \frac{2}{3}(1 + 1)(1) = \frac{4}{3} \quad (3.12)$$

$$V_C(\infty) = \frac{2}{3} \quad (3.13)$$

```
wget https://github.com/Pranavb060504/
SignalProcessing/blob/main/
circuits_and_transforms/vt1.py
```